



---


# MEMS1082

## Chapter 6 Digital Circuit 6-4


 
# Sequential Logic


- ◆ Sequential logic devices usually respond to inputs when a separate trigger signal transitions from one level to another.
- ◆ The trigger signal is referred to as the **Clock (CK)** signal.




 
# Flip-Flops

- ◆ Flip-flops is called a bi-stable device, since it has only two possible stable output states: 1 (high) and 0 (low).
- ◆ It has the capability of remaining in a particular state until input signal cause it to change.
  - **S** is the **SET** input, **R** is **RESET** input
  - **Q** and  $\bar{Q}$  are the **complementary** outputs




1. As long as the inputs  $S$  and  $R$  are both 0, the outputs of the flip-flop remain unchanged.
2. When  $S$  is 1 and  $R$  is 0, the flip-flop is *set* to  $Q = 1$  and  $\bar{Q} = 0$ .
3. When  $S$  is 0 and  $R$  is 1, the flip-flop is *reset* to  $Q = 0$  and  $\bar{Q} = 1$ .
4. It is “not allowed” (NA) to place a 1 on  $S$  and  $R$  simultaneously since the output will be unpredictable.



# Flip-Flops

- ◆ A flip-flop circuit can be constructed from two NAND gates or two NOR gates.
- ◆ Flip-flop has two outputs,  $Q$  and  $\bar{Q}$ , and two inputs, *set* and *reset*. This type of flip-flop is referred to as an ***SR flip-flop*** or ***SR latch***.
 
## Basic flip-flop circuit with NOR gates



S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(after S=1, R=0)


(after S=0, R=1)

NA



# Flip-Flops
 
## Basic flip-flop circuit with NAND gates (NAND latch)




S	R	Q	$\bar{Q}$
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

← NA



 
# Basic flip-flop circuit with NAND gates

NAND latch has two possible resting states when  $SET = CLEAR = 1$ .




After  $S=1, R=0$

 


After  $S=0, R=1$

# Basic flip-flop circuit with NAND gates

**Figure** Pulsing the SET input to the 0 state will always produce the  $Q = 1, \bar{Q} = 0$ :  
output state (a)  $Q = 0$  prior to SET pulse; (b)  $Q = 1$  prior to SET pulse.

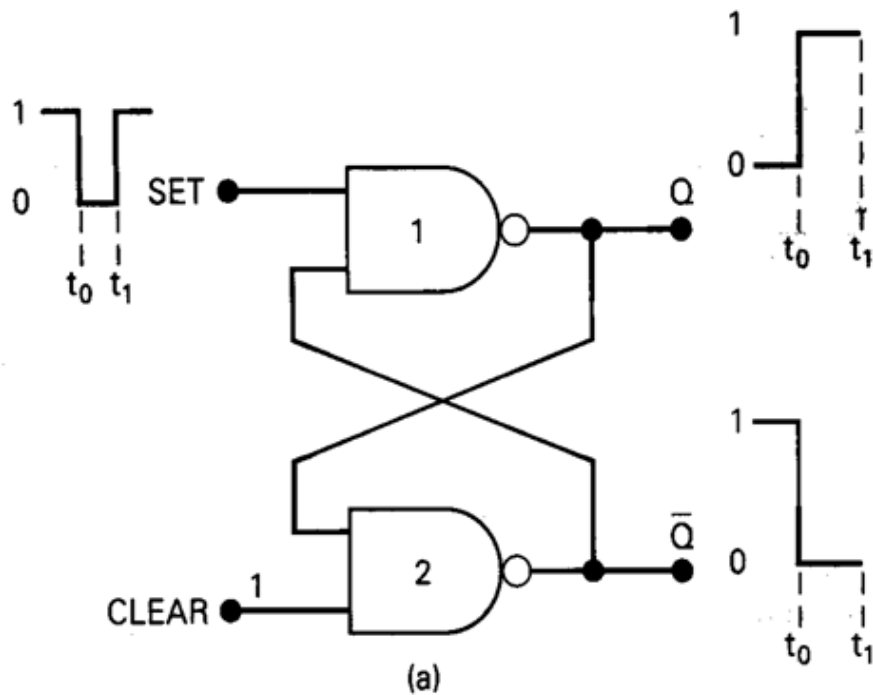

R


 


R

# Basic flip-flop circuit with NAND gates


**Figure** Pulsing the  $\overline{\text{CLEAR}}$  input to the LOW state will always produce  $Q = 0$ ,  $\overline{Q} = 1$ :

 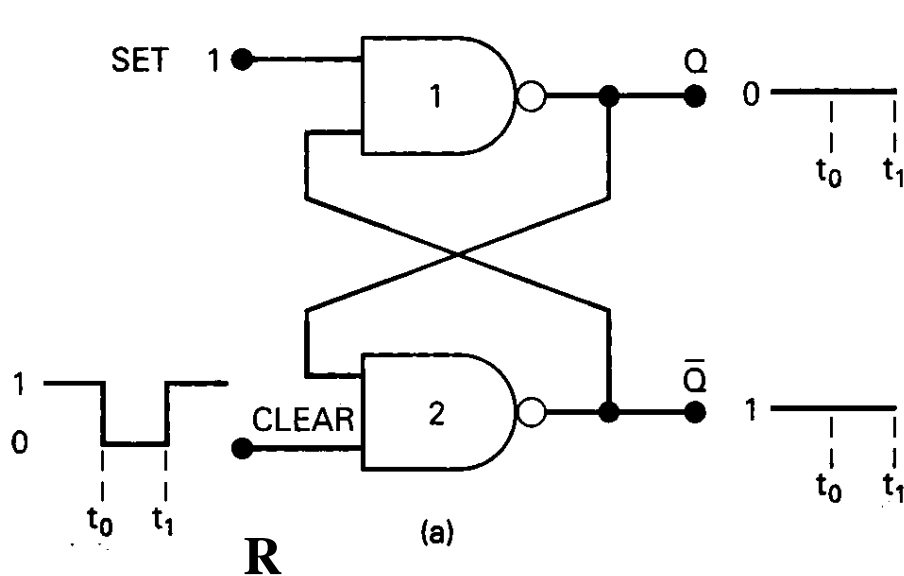(a)  $Q = 0$  prior to  $\overline{\text{CLEAR}}$  pulse; (b)  $Q = 1$  prior to  $\overline{\text{CLEAR}}$  pulse.




 
# Basic flip-flop circuit with NAND gates



Set	Clear	Output
1	1	No change
0	1	$Q = 1$
1	0	$Q = 0$
0	0	Invalid*

\*produces  $Q = \bar{Q} = 1$

(b)

(a) NAND latch; (b) truth table.

# Flip-Flops

## ◆ Truth Table for the RS Flip-flop


 


Table 6.4 Truth table for the RS flip-flop

Inputs		Outputs	
$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q_0$	$\bar{Q}_0$
1	0	1	0
0	1	0	1
1	1	NA	

Compare with

 

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0


(after S=1, R=0)

(after S=0, R=1)


← NA
 
# Flip-Flops

- ◆ RS flip-flop internal design and timing



(a) internal design

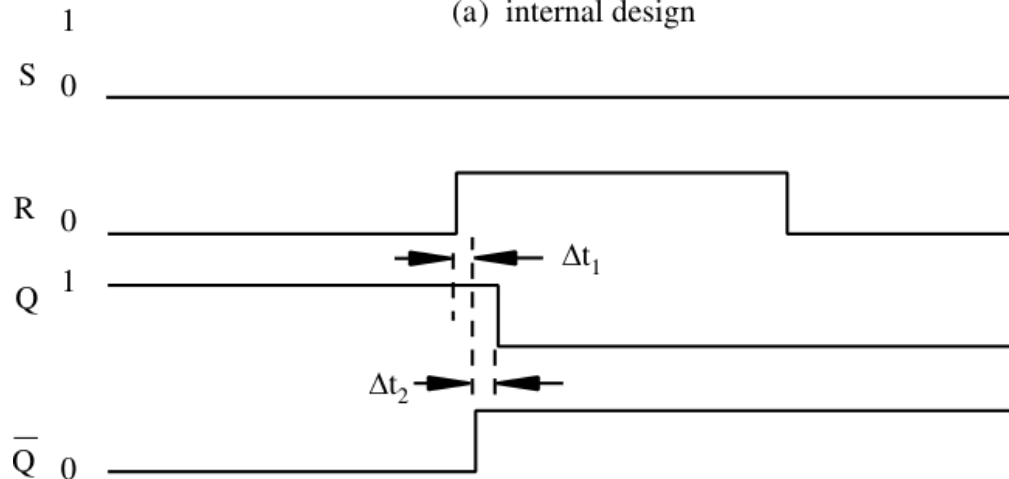


(b) timing diagram


 
# Triggering of Flip-Flops


- ◆ The clocked SR flip-flop consists of a basic NOR flip-flop and two AND gates. The outputs of the two AND gates remain at 0 as long as the clock pulse (or CP) is 0, regardless of the S and R input values. When the clock pulse goes to 1 (positive-edge transition), information from the S and R inputs passes through to the basic flip-flop. With both S=1 and R=1, the occurrence of a clock pulse causes both outputs to momentarily go to 0. When the pulse is removed, the state of the flip-flop is indeterminate, i.e., either state may result, depending on whether the set or reset input of the flip-flop remains a 1 longer than the transition to 0 at the end of the pulse.




Q	S	R	Q(t+1)	↑ CK
0	0	0	0	
0	0	1	0	
0	1	0	1	
0	1	1	indeterminate	
1	0	0	1	
1	0	1	0	
1	1	0	1	
1	1	1	indeterminate	



# Edge-triggered RS flip-flops

 

(a) positive edge-triggered

 

(b) negative edge-triggered

 



Table 6.5 Positive edge-triggered RS flip-flop truth table

$S$	$R$	$CK$	$Q$	$\bar{Q}$
0	0	$\uparrow$	$Q_0$	$\bar{Q}_0$
1	0	$\uparrow$	1	0
0	1	$\uparrow$	0	1
1	1	$\uparrow$	NA	
X	X	0, 1	$Q_0$	$\bar{Q}_0$

As long as no positive edge transition



# Edge-triggered RS flip-flops

 


Positive edge-triggered RS flip-flop timing diagram.

1. If  $S$  and  $R$  are both 0 when the clock edge is encountered, the output state remains unchanged.
2. If  $S$  is 1 and  $R$  is 0 when the clock edge is encountered, the flip-flop output is **set** to 1. If the output is at 1 already, there is no change.
3. If  $S$  is 0 and  $R$  is 1 when the clock edge is encountered, the flip-flop output is **reset** to 0. If the output is at 0 already, there is no change.
4.  $S$  and  $R$  should never both be 1 when the clock edge is encountered.
 
# Latch-not edge triggered device


- ◆ Output Q tracks the input D as long as CK is high
  - Transparent when CK is high



Latch.

**Table 6.6** Latch truth table


$D$	$CK$	$Q$	$\bar{Q}$
0	1	0	1
1	1	1	0
X	0	$Q_0$	$\bar{Q}_0$

 

Latch timing diagram.

# Asynchronous inputs

 - ◆ Preset and clear functions to override any inputs... called asynchronous inputs
- ◆ Present is to set the output  $Q$  to high (1), clear input is to set the output  $Q$  to low


 


**Figure 6.12** Preset and clear flip-flop functions.

 

# D Flip-Flops

- The D flip-flop is a modification of the clocked SR flip-flop. The D input goes directly into the S input and the complement of the D input goes to the R input. The D input is sampled during the occurrence of a clock pulse. If it is 1, the flip-flop is switched to the set state (unless it was already set). If it is 0, the flip-flop switches to the clear state.



Positive edge-triggered D flip-flop.

**Table 6.7** Positive edge-triggered D flip-flop truth table


$D$	$CK$	$Q$	$\bar{Q}$
0	$\uparrow$	0	1
1	$\uparrow$	1	0
X	0	$Q_0$	$\bar{Q}_0$
X	1	$Q_0$	$\bar{Q}_0$

$Q$	$D$	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1


 
# JK Flip-Flop

- ◆ A JK flip-flop is a refinement of the SR flip-flop in that the indeterminate state of the SR type is defined in the JK type. Inputs J and K behave like inputs S and R to set and clear the flip-flop .
- ◆ J is for set and the letter K is for clear.
- ◆ When logic 1 inputs are applied to both J and K simultaneously, the flip-flop switches to its complement state, i.e., if  $Q=1$ , it switches to  $Q=0$  and vice versa.
- ◆ Output Q is ANDed with K and CP inputs so that the flip-flop is cleared during a clock pulse only if Q was previously 1. Similarly, output Q' is ANDed with J and CP inputs so that the flip-flop is set with a clock pulse only if Q' was previously 1.




Transition table

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0



# JK Flip-Flop

 

Negative edge-triggered JK flip-flop.

**Table 6.8** Truth table for a negative edge-triggered JK flip-flop

$\overline{\text{Preset}}$	$\overline{\text{Clear}}$	CK	J	K	Q	$\overline{Q}$
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0			NA		
1	1	$\downarrow$	0	0	$Q_0$	$\overline{Q_0}$
1	1	$\downarrow$	1	0	1	0
1	1	$\downarrow$	0	1	0	1
1	1	$\downarrow$	1	1	$\overline{Q_0}$	$Q_0$
1	1	0, 1	X	X	$Q_0$	$\overline{Q_0}$


# JK Flip-Flop

**Table 6.9** Positive edge-triggered T flip-flop truth table

T	$\overline{\text{Preset}}$	$\overline{\text{Clear}}$	$Q$	$\overline{Q}$
$\uparrow$	1	1	$\overline{Q}_0$	$Q_0$
0	1	1	$Q_0$	$\overline{Q}_0$
1	1	1	$Q_0$	$\overline{Q}_0$
X	0	1	1	0
X	1	0	0	1

T (toggle) flip-flop


Toggle: the output changes to opposite state

 


**Figure 6.15** Positive edge-triggered T flip-flop.
 
# Switch circuits

- ◆ Logic described previously can be implemented as an actual circuit. Switches are left open for logic 0 and closed for logic 1.
- ◆ Two variable AND circuit  $X \cdot Y$




- ◆ Two variable OR circuit  $X + Y$

 

# Switch circuits

- ◆ Four variable circuit  $UV(X + Y)$

 



# AND Gate

AND gate

AND logic



$$C = A \cdot B$$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


- ◆ Two input AND gate using "diode-resistor" logic is shown in figure below, where X, Y are inputs and F is the output.

If X = 0 and Y = 0, then both diodes D1 and D2 are forward biased and thus both diodes conduct and pull F low.

If X = 0 and Y = 1, D2 is reverse biased, thus does not conduct. But D1 is forward biased, thus conducts and thus pulls F low.

If X = 1 and Y = 0, D1 is reverse biased, thus does not conduct. But D2 is forward biased, thus conducts and thus pulls F low.

 If X = 1 and Y = 1, then both diodes D1 and D2 are reverse biased and thus both the diodes are in cut-off and thus there is no drop in voltage at F. Thus F is HIGH.





# OR Gate

OR gate

OR logic



$$C = A + B$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


Two input OR gate using "diode-resistor" logic is shown in figure below, where X, Y are inputs and F is the output:

If  $X = 0$  and  $Y = 0$ , then both diodes D1 and D2 are reverse biased and thus both the diodes are in cut-off and thus F is low.

If  $X = 0$  and  $Y = 1$ , D1 is reverse biased, thus does not conduct. But D2 is forward biased, thus conducts and thus pulling F to HIGH.

If  $X = 1$  and  $Y = 0$ , D2 is reverse biased, thus does not conduct. But D1 is forward biased, thus conducts and thus pulling F to HIGH.

 If  $X = 1$  and  $Y = 1$ , then both diodes D1 and D2 are forward biased and thus both the diodes conduct and thus F is HIGH.








# NOT Gate

Inverter  
(INV, NOT)

Invert signal  
(complement)

 

$$C = \bar{A}$$

A	C
0	1
1	0

NOT gate using "transistor-resistor" logic is shown in the figure below, where X is the input and F is the output.

When  $X = 1$ , The transistor input pin 1 is HIGH, this produces the forward bias across the emitter base junction and so the transistor conducts. As the collector current flows, the voltage drop across  $R_L$  increases and hence F is LOW.

When  $X = 0$ , the transistor input pin 2 is LOW: this produces no bias voltage across the transistor base emitter junction. Thus Voltage at F is HIGH.

