


3

input device
pressed \Rightarrow low
released \Rightarrow high

display:

high \Rightarrow lit
low \Rightarrow dark

L Low = 0V
H HIGH = 5V

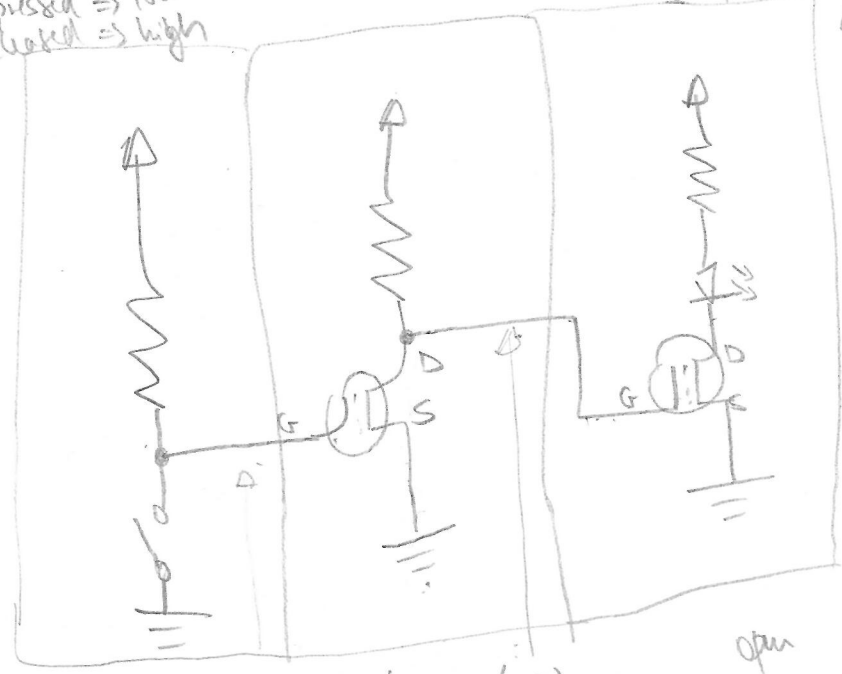


released open
pushed closed

High
Low

open

Low
High

open dark
closed lit

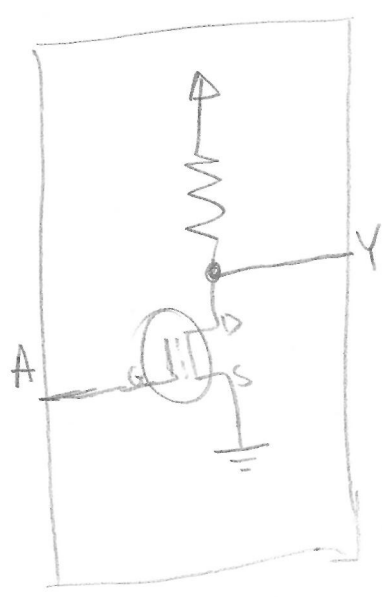

A	Y
L	H
H	L

$$Y = \text{Not } A$$

$$Y = \bar{A}$$

NOT
inverter

!

